
ELECTRIC CIRCUITS


Name: _____

PHYSICAL SCIENCE

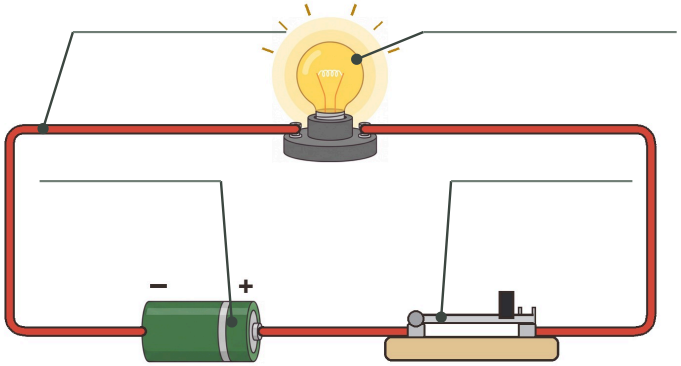
Write the name of each part on its line. Use the word bank.




_____

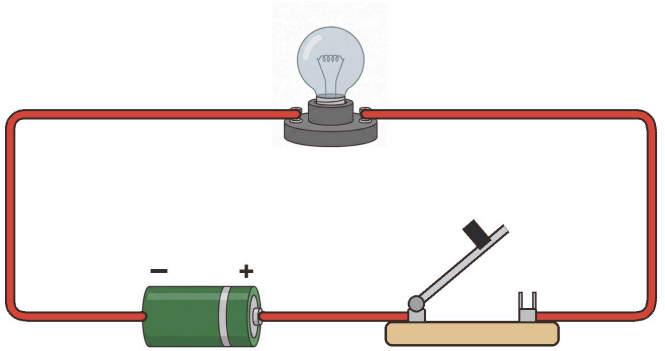

_____

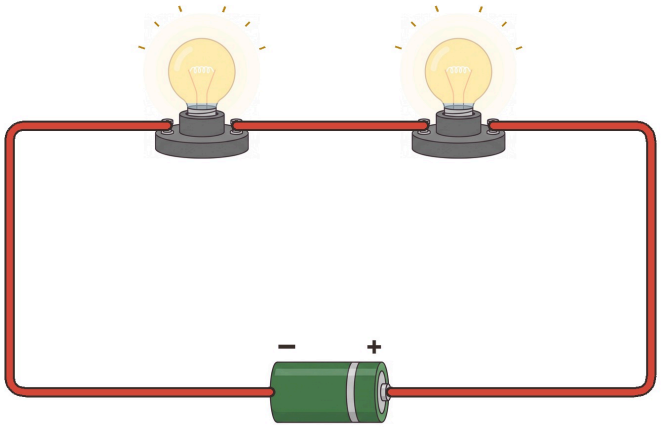

_____

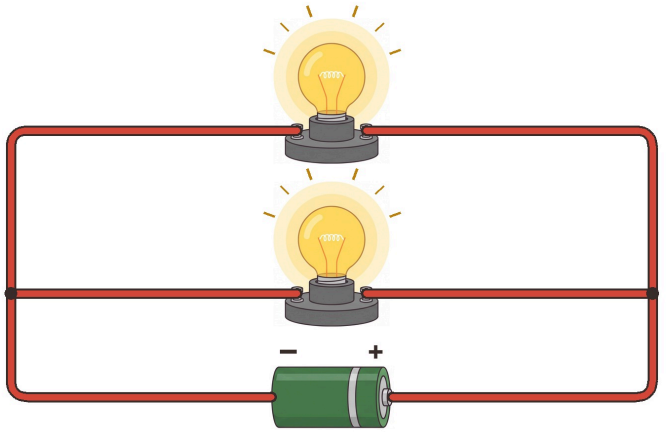


_____


Word bank Battery Closed circuit Light bulb Open circuit Parallel circuit Series circuit Switch Wire

ELECTRIC CIRCUITS


PHYSICAL SCIENCE *Answer key*

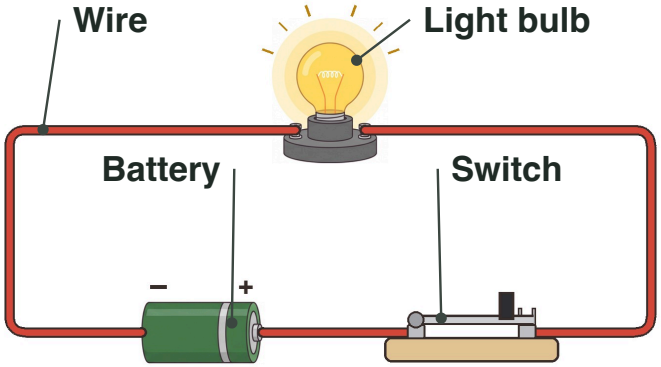


Closed circuit

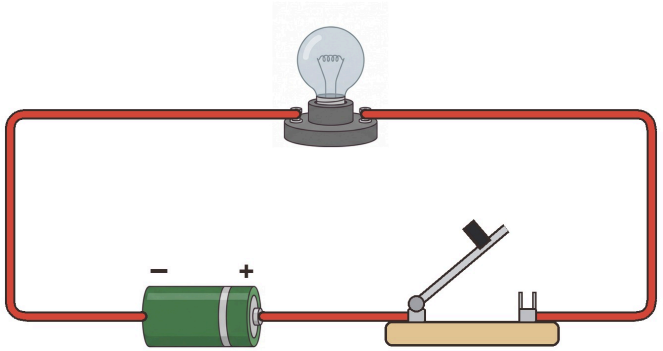

Open circuit

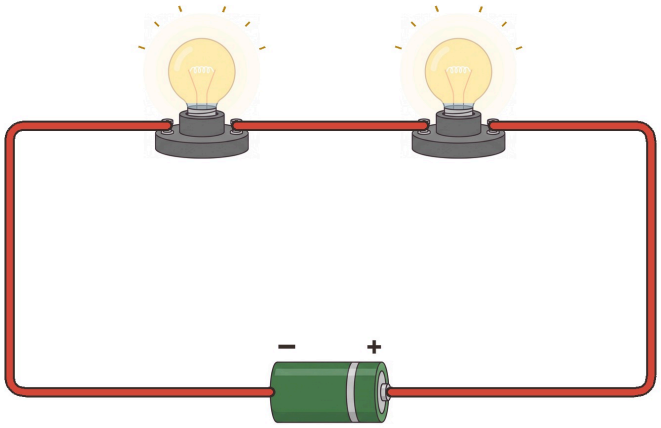

Series circuit

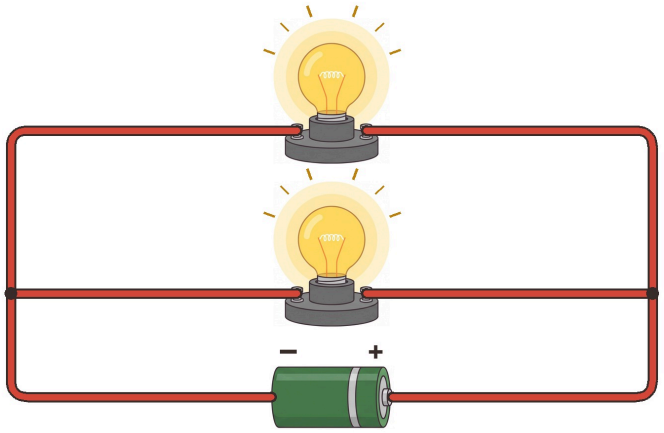

Parallel circuit